



Final-Term Exam of (Electrical Machines I)  
For 2<sup>nd</sup> Grad Electrical Engineering Dept. students.

الإمتحان من جزأين: من فضلك أجب كل جزء من الإمتحان في اتجاه مختلف من ورقة الإجابة.

Answer the following questions and assume any missing data:

**Part (I)**

**Question No (1): (5+10 Marks)**

1-1) **Numerate** the different types of dc. machines? **Draw** the circuit diagram and **write** the voltage equation of each type as motor and generator and **compare** their external characteristics.

1-2) **Calculate** the ampere-turns required for the tooth of dc. armature with the following dimensions:

Armature diameter = 656.3 mm;

No of slots = 72 slots;

Core-outer diameter = 634.3 mm;

Slot-width = 10 mm with parallel sides;

Slot pitch flux = 10.715 mWb

Armature gross length = 350 mm;

No of ventilating ducts = 5 each 1 cm wide;

Iron space factor = 0.89.

The magnetization B-H curve for the material used is given by:

$$B = 3.77 \times 10^4 H^4 - 2.86 \times 10^5 H^3 + 8.12 \times 10^5 H^2 - 1.03 \times 10^6 H + 4.86 \times 10^5$$

**Question No (2): (5+10 Marks)**

2-1) **Explain** clearly the reasons for the fall in terminal voltage of a dc. shunt generator as it is loaded. **What** modifications are necessary to compensate the voltage drop due to load and feeder?

2-2) The following data pertain to the magnetization curve of a D.C. shunt generator at 1500 r.p.m.

I <sub>f</sub> [A]	0	0.4	0.8	1.2	1.6	2.0	2.4	2.8	3.0
E <sub>a</sub> [V]	6	60	120	172.5	202.5	221	231	237	240

For this generator, **obtain**:

- The voltage on open circuit which the machine will build up for a total shunt field resistance of 100 Ω.
- The critical value of shunt field resistance at 1500 r.p.m.
- The critical speed for the shunt field resistance of 100 Ω.
- The terminal voltage of the generator if the total armature resistance is 0.3 Ω, armature current is 50 A and the speed is 1500 r.p.m. Neglect armature reaction.
- The external characteristic, maximum armature current and short circuit current.

**Question No (3): (5+5+5 Marks)**

3-1) **Discuss** the power flow inside dc machine, and deduce the efficiency equation. At what load does maximum efficiency occur?

3-2) **Draw** a neat diagram of a three-point starter, **label** its parts, and explain how it works. Also **explain** its defect and the protective devices therein.

3-3) A 4-pole, 250 V, 7.5 KW (output), wave-connected shunt motor has an armature resistance of 0.4 Ω and a field resistance of 125 Ω. **Estimate** the current taken by the motor on no-load if the full-load efficiency of the motor is 86%.

## Mansoura University

Faculty of Engineering  
Electrical Eng. Dept.

Second Year Exam.  
Time: 1.5 Hours

"ELECTRIC MACHINE FINAL-TERM EXAM PART (1)-2013"

### ANSWER FOUR QUESTIONS OF THE FOLLOWING:

- 1) (a) From the principle derive the transformer equivalent circuit parameters.  
(b) A 20 KVA, 2200/220 V, 50 Hz, single-phase transformer has the following equivalent circuit parameters referred to the high potential terminals of the transformer.  $R_1 = 2.51 \Omega$ ,  $R_2 = 3.11 \Omega$ ,  $X_m = 25100 \Omega$ ,  $X_1 = 10.9 \Omega$ ,  $X_2 = 10.9 \Omega$ .
- The transformer is supplying 15 KVA, 220 Volt at lagging power factor of 0.85. Draw the approximate equivalent circuit with its parameter values and determine;
- the primary potential difference required;
  - the power factor at the primary terminals ;
  - the transformer maximum regulation ;
  - the transformer maximum efficiency if the constant losses = 900 watt ;
  - draw the vector diagram with voltage scale 1:100 . [14 pts]
- 2) (a) Draw the magnetizing current waveforms at no-load during the transient and steady-state periods. Derive the expression required to explain its nonlinearity.  
(b) Three 10 KVA, 1330/250 V, 50 Hz single-phase transformers are connected in star/delta to form 3-phase transformer bank to supply at 250 volts line-to-line a heating load of 2 KW per phase and a three-phase load of 23 KVA at 0.8 lagging power factor. Determine the line current supplying the transformers, and the voltage regulation in the following both cases;
- the three single-phase transformers are considered ideal;
  - each one of the three single-phase transformer impedance is  $0.118 + j0.238$  referred to low-potential side. However, the loads are connected to the 3-phase transformers bank by means of a common three-phase feeder whose impedance is  $0.003 + j0.010 \Omega$  per phase. Moreover, the 3-phase transformers bank themselves are supplied from a constant-potential source by means of a three-phase feeder whose impedance is  $0.75 + j5.0 \Omega$ , per phase. [14 pts]
- 3) (a) Discuss and derive all the expressions required to illustrate the transformer operation under the variable frequency source.  
(b) the equivalent circuit parameters of the audio transformer are as following:  
 $R_1 = 4 \Omega$ ,  $R_2 = 0.40 \Omega$ ,  $L_m = 35 \text{ mH}$ ,  $L_{11} = 0.4 \text{ mH}$ ,  $L_{12} = 0.045 \text{ mH}$ ,  
 $N_1/N_2 = 5$ .
- The speaker resistive load =  $4 \Omega$  is connected to the transformer