

## Final Term Exam June 2011

Answer the following Questions


Total Marks= 60

### First Question (10 Marks)

- a) **Explain** with the help of neat sketch the components of a generalized model of any instrument. **Clarify** the function of each component in the instrumentation process (5 marks)
- b) **Explain FIVE ONLY** of the following terms:  
"calibration", "interfering inputs", "random errors", "passive sensors", "accuracy", "damping torque", and "sensor fusion" (5 marks)

### Second Question (10 Marks)

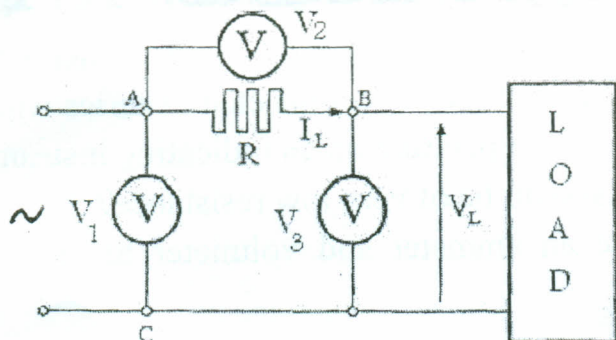- a) **Explain** briefly the main errors of wattmeters and the methods used to overcome each of them. (5 marks)
- b) The circuit shown can be used to measure the power and power factor of the connected load. **Evaluate** the expression that can be used to compute both the power and power factor. **Draw** the vector diagram of the circuit. (5 marks)



### Third Question (10 Marks)

- a) **Describe briefly** (with the help of neat diagram) the construction and the principle of operation of the dc galvanometer. **State** the methods used to improve the sensitivity of the galvanometers. (5 marks)
- b) A moving coil voltmeter with resistance of 20 ohm gives full scale deflection of  $120^\circ$  when a potential difference of 100 mV is applied across it. The moving coil has dimensions of 30mm\*25mm and is wound with 100 turn. The spring constant is  $0.375 \times 10^{-6}$  Nm/deg. **Find** the flux density in the air gap. **Find also** the diameter of copper wire of coil winding if 30% of instrument resistance is due to coil winding ? for copper =  $1.7 \times 10^{-8}$  ohm.m? (5 marks)

الأسئلة من صفحتين من فضلك اقلب الورقة

### Fourth Question (10 Marks)

- 4-a) **Explain** with the help of neat sketch, the construction and operating principle of a current transformer. **Why** it is essential to shorten the secondary of the current transformer is not connected to a load (5 marks)
- 4-b) **Explain** with the help of neat sketch the use of internal resistances to change the range of reading of both a moving coil voltmeter and a moving coil ammeter. (5 marks)

### Fifth Question (10 Marks)

- 5-a) **Explain** the construction of a Permanent Magnet Moving Coil (PMMC) meter with the help of neat sketch. How are different forces produced? Enlist the advantages and disadvantages of PMMC meters (5 marks)
- 5-b) Two wattmeters are connected to measure the power in 3 phase 3 wire balanced system gave readings of 5000 W and 1000 W .
- Draw** a schematic diagram of the system connection.
  - Calculate** the power and the power factor if:
    - both meters read direct, and
    - the second meter has to be reversed. (5 marks)

### Sixth Question (10 Marks)

- 6-a) **Give SHORT** answer of **FOUR ONLY** of the following questions: (4 marks)  
أجب باختصار على أربعة فقط من الأسئلة التالية مع كتابة رقم السؤال كما هو في ورقة الأسئلة:
- What is the function of electrical measuring instruments?
  - What happen when a voltmeter is connected in series with the circuit?
  - What is the effect of temperature on an indicating instrument?
  - Why an ammeter should be of very low resistance?
  - Is it right to use an ammeter and voltmeter to measure power in ac circuits? Why?
- 6-b) The four arms of an alternating current bridge are made up as follows:
- arm ab** : an imperfect capacitor  $C_1$  with an equivalent series resistance of  $r_1$ ;
  - arm bc** : a non inductive resistance  $R_3$  ;
  - arm cd** : a non inductive resistance  $R_4$  ;
  - arm da** : an imperfect capacitor  $C_2$  with an equivalent resistance of  $r_2$  in series with a resistance  $R_2$ .
- A supply of 450 Hz is given between terminal **a** and **c**, and the detector is connected between **b** and **d**.
- Evaluate** expressions for  $C_1$  and  $r_1$  to give balance.
  - Calculate** the values of  $C_1$  and  $r_1$  at balance for:  $R_2 = 4.8 \Omega$ ;  $R_3 = 2000 \Omega$ ;  $R_4 = 2850 \Omega$ ;  $C_2 = 0.5 \mu F$  and  $r_2 = 0.4 \Omega$ . (6 marks)

*With my Best Wishes*

*Prof. Magdi El-Saadawi*

16/6/2011