

Answer the following questions

Q1) Determine V_o for the circuits shown in Fig.1

Q2)(a) Why we must use Zener diode in the power supply circuits?

(b) Determine the range of values of V_i that will maintain the Zener diode of Fig.2 in the "ON" state.

Q3)(a) Why the voltage divider bias is the best one for the BJT DC bias ?

(b) Make the DC analysis for the circuit shown in Fig. 3

Q4)Design an emitter stabilization circuit for a BJT at $I_{CQ} = 0.5 I_{Csat}$,

$V_{CEQ} = 0.5 V_{cc}$, if $V_{cc} = 20 \text{ V}$, $I_{Csat} = 10 \text{ mA}$, $\beta = 100$,and $R_E = 4 \text{ k}\Omega$.

Q5)(a) What are the advantages of FET and BJT?

(b) Explain the n-channel enhancement MOSFET.

Q6) Determine I_{DQ} , V_{GSQ} , V_D , V_s , V_{DS} , V_{DG} for the circuit shown in Fig.4.

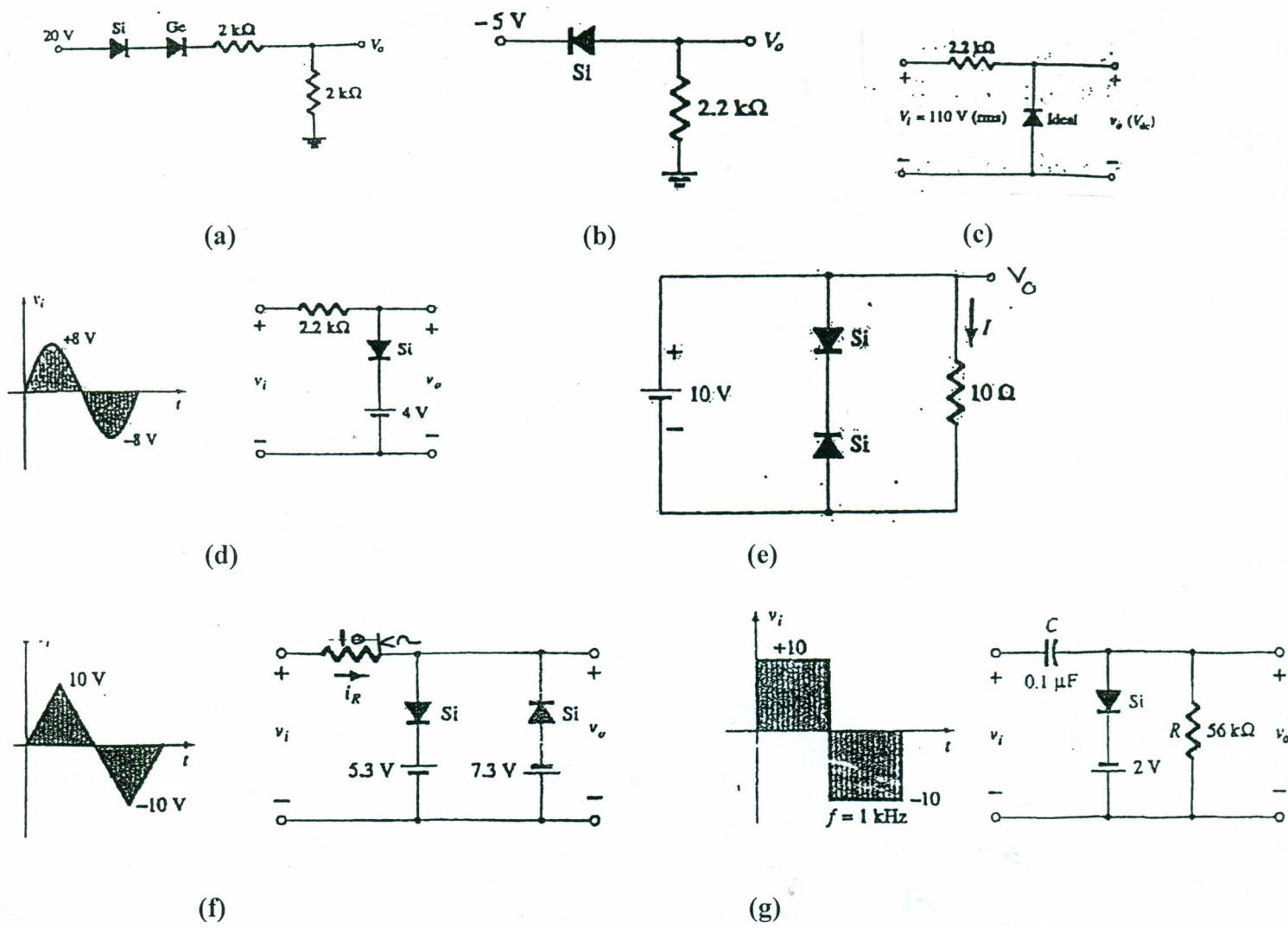


Fig.1

