



**Part I [50 Marks]**

**Question (1): [Marks 21]**

- (a) Deduce the Bode plot ( $V_{dB}$ ,  $\theta$ ) for a low-pass filter [Marks 7] [ILO's a4.3,b2.3 ]
- (b) Design an R- C high-pass filter to have a cutoff frequency of 500 Hz using a resistor of 1.2 K $\Omega$  . Then sketch the resulting magnitude and phase plot for a frequency range of 0.1  $f_c$  to 10  $f_c$ . Also, if the input voltage to the filter is 20  $\angle 0^\circ$  V, using the sketches , find the output voltage of the filter if the input frequencies are 100 Hz , 500 Hz, and 1000 Hz. [Marks 7] [ILO's b2.2 ]
- (c) Determine the following for the pulse waveform of Fig. 1
- |                               |                      |                |              |
|-------------------------------|----------------------|----------------|--------------|
| a) Positive or negative going | b) base-line voltage | c) pulse width | d) amplitude |
| e) % tilt                     | f) the average value | [ Marks 7 ]    |              |

[ ILO's a13.2 ]

**Question (2): [Marks 15]**

- (a) Deduce the expressions for the input and output impedances of the Z- parameter equivalent circuit. [Marks 7] [ILO's a4.1,b1.1,c1.1 ]
- (b) Determine the admittance (Y) parameters for the network of Fig. (2) [Marks 8]  
 [ILO's b1.2,c1.3 ]

**Question (3): [Marks 14]**

- (a) Two impedances  $Z_1$  and  $Z_2$  are connected in parallel across a 200 V, 50 Hz supply, the impedance  $Z_1$  consists of 30  $\Omega$  resistance in series with 30  $\Omega$  inductive reactance while the impedance  $Z_2$  consists of a variable resistance in series with 25  $\Omega$  capacitive reactance. Draw the locus diagram of the total current and determine the resistance of  $Z_2$  for which the current is in resonance. [Marks 7]  
 [ILO's c1.3 ]
- (b) Obtain the equivalent mechanical equation for the electrical system shown in Fig. 3 [Marks 7]  
 [ILO's a1-1,c1-1 ]

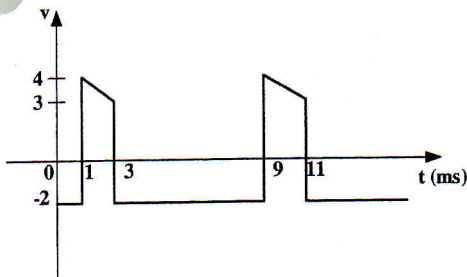


Fig.1

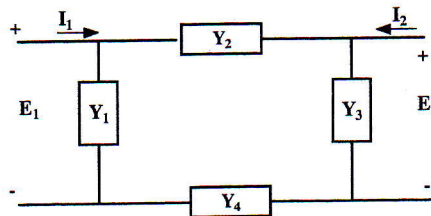


Fig.2

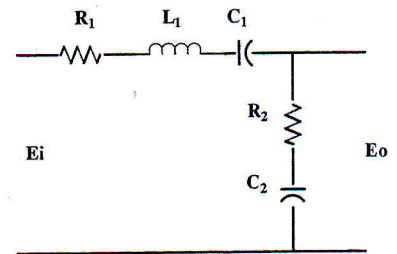


Fig.3

## Part II

**Question (4)** ( 15 marks ) [ ILO's 24.3, b2.3 ]





- (a) Determine the sum of the following two non-sinusoidal voltage waveforms :-  
 $V_1 = 30 + 20 \sin(20t) + 5 \sin(60t + 30)$   
 $V_2 = 50 + 10 \sin(20t) + 30 \sin(40t) + 10 \cos(60t)$
- (b) For the network of Fig.(4-b), determine :-  
 1- the sinusoidal expression for the voltage  $V_3$   
 2- sketch  $V_3$  and calculate its r.m.s value

**Question (5)** ( 15 marks ) [ ILO's b.11, c1.3 ]

- (a) Using format approach to nodel analysis, find the voltage across the 4 Ohms resistor in Fig( 5-a).  
 (b) Using mesh analysis , find the current through the 10 K $\Omega$  resistor in Fig.(5-b)

**Question (6)** ( 20 marks ) [ ILO's 24.1, b1.1, c.1.1 ]

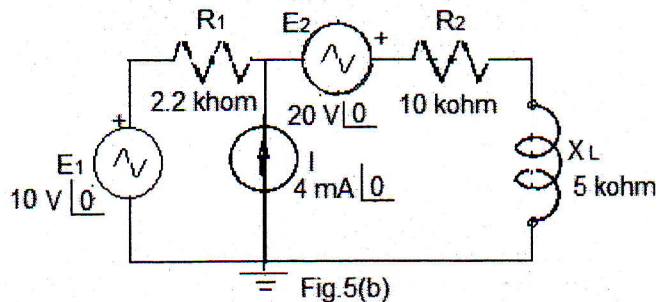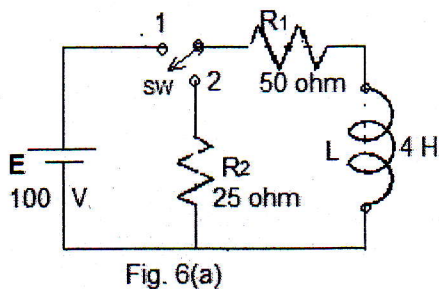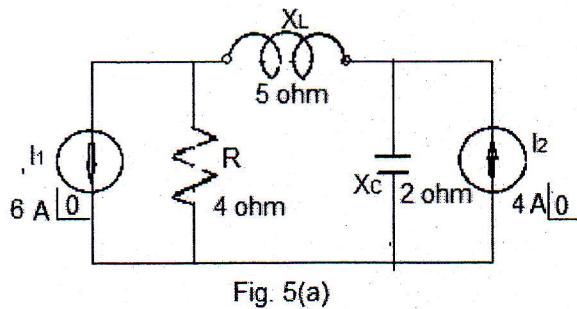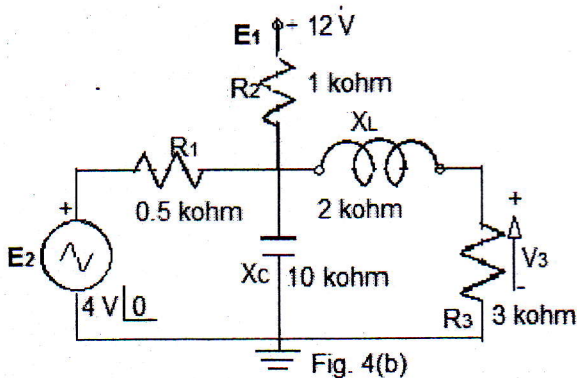- (a) In the circuit shown in Fig. (6-a), the switch has been closed in position (1) for long time to establish the steady state current . When the switch is moved to position(2), a transient current exists in the two resistors for a short time . Determine :-  
 1-the current after 40 msec.  
 2-the energy dissipated in the resistors ( $R_1$  ,  $R_2$  )  
 3-sketch  $i_L$ ,  $v_L$ ,  $v_{R1}$ , and  $v_{R2}$  against time.
- (b) RC series circuit with  $R=100$  Ohms and  $C=25 \mu F$  has a sinusoidal voltage source  $V=250 \sin(500t)$  Volts. Assuming there is no-initial charge on the capacitor, find:-  
 1- A mathematical expression for the circuit current.  
 2- How many cycles will occur during the transient period



**With best wishes**