
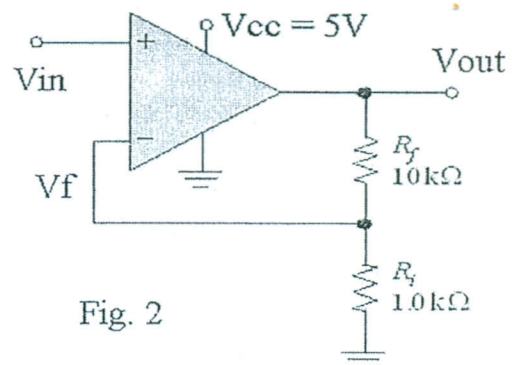


Answer the following 25 MCQs in the MCQ answer sheet in the answer booklet:

(for each correct answer, you get 3 marks for a total of 75 Marks)

(for each wrong answer, you get -1 mark) & (You get zero for unanswered questions)

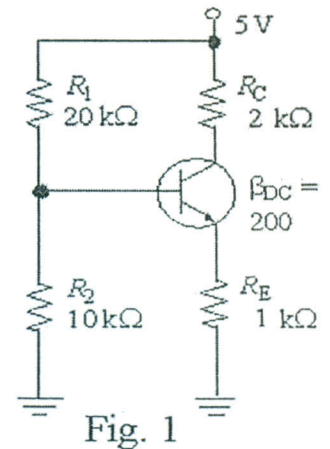- Q1 When a BJT is in saturation, the
- ① base current cannot increase
 - ② collector to emitter voltage is maximum
 - ③ collector current does not change with an increase in base current
 - ④ None of the above
- Q2 In Fig. 1, the dc load line will intersect the y-axis at
- ① 1 mA
 - ② 2.5 mA
 - ③ 1.67 mA
 - ④ 5 mA
- Q3 If you Thevenize the input voltage divider, the Thevenin resistance is
- ① 6.67 k Ω
 - ② 10 k Ω
 - ③ 20 k Ω
 - ④ 30 k Ω
- Q4 A well-designed CC amplifier has
- ① current gain > 1
 - ② voltage gain > 1
 - ③ both of the above
 - ④ none of the above
- Q5 The efficiency of a class A output stage amplifier is
- ① close to 100%
 - ② around 75%
 - ③ about 50%
 - ④ less than 25%
- Q6 The conduction angle of the transistor of a class B output stage amplifier equals
- ① 90°
 - ② between 90 & 180°
 - ③ 180°
 - ④ 270°
- Q7 A class AB amplifier is designed to operate in the linear region
- ① for the whole input cycle
 - ② for slightly more than 1/2 of the input cycle
 - ③ for exactly 1/2 of the input cycle
 - ④ for slightly less than 1/2 of the input cycle
- Q8 Crossover distortion (dead-zone) is present in
- ① class A output stage amplifier
 - ② class B output stage amplifier
 - ③ class AB output stage amplifier
 - ④ none of the above
- Q9 The gain of the OP AMP shown in Fig. 2 is
- ① -10
 - ② 1
 - ③ 10
 - ④ 11
- Q10 For the OP AMP in Fig.2: If $V_{in} = 1V$, the approximate value of V_{out} is
- ① -1V
 - ② -10V
 - ③ 5V
 - ④ 11V




Q11 The input impedance of a noninverting amplifier is

- ① nearly 0 ohms
- ② approximately equal to R_i
- ③ approximately equal to R_f
- ④ extremely large

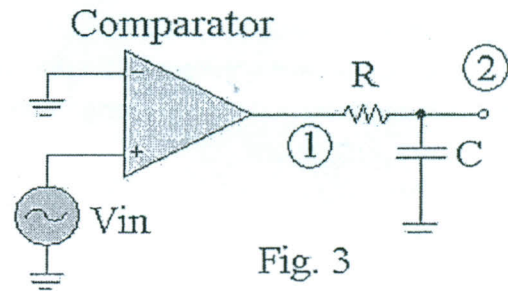Q12 In Fig. 3: the signal at node 1 is

- ① DC level
- ② square wave
- ③ triangle wave
- ④ series of +ve and -ve pulses



Q13 In Fig. 3: the signal at node 2 is

- ① DC level
- ② square wave
- ③ triangle wave
- ④ series of +ve and -ve pulses

Q14 Hysteresis is incorporated in a comparator by adding

- ① a capacitor in series with the input
- ② capacitors from the power supply to ground
- ③ a small resistor in series with the input
- ④ positive feedback

Q15 A comparator output can be limited (bounded) by

- ① reversing the power supply voltages
- ② decreasing the input resistance
- ③ putting a zener diode in a feedback path
- ④ connecting the inverting input to ground

Q16 When an instrumentation amplifier uses guarding, the shield is driven by a

- ① low-impedance differential source
- ② low-impedance common-mode source
- ③ high-impedance differential source
- ④ high-impedance common-mode source

Q17 A typical instrumentation amplifier has

- ① high CMRR
- ② unity gain
- ③ low input impedance
- ④ all of the above

Q18 An application where an isolation amplifier is particularly useful is when


- ① the input signal has very large dynamic range
- ② control of the freq. response is necessary
- ③ voltages could present a hazard
- ④ all of the above


Q19 The filter in Fig. 4 is a

- ① low-pass filter
- ② high-pass filter
- ③ band-pass filter
- ④ notch filter

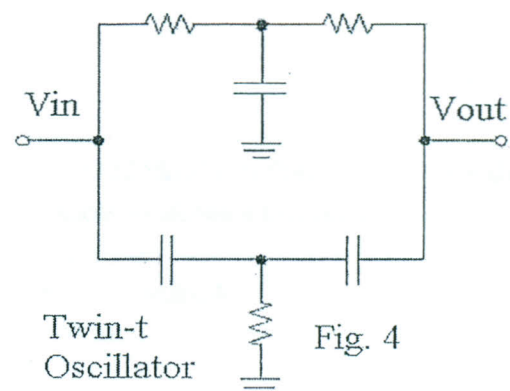Q20 An example of an LC feedback oscillator is a

- ① Colpitts oscillator
- ② Wien-bridge oscillator
- ③ phase-shift oscillator
- ④ relaxation oscillator



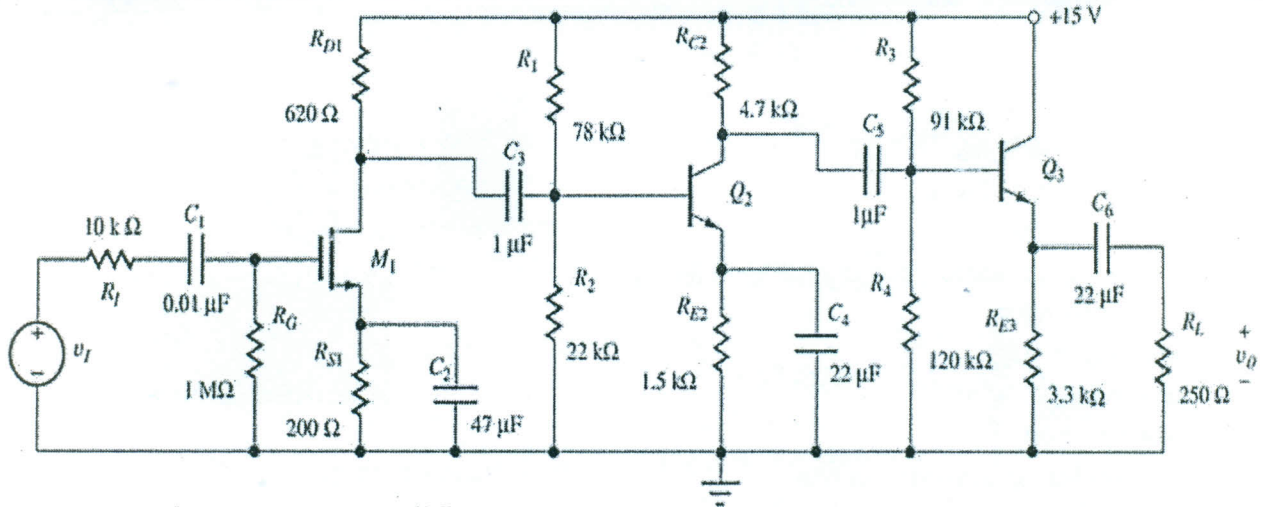

Three-stage amplifier

AC equivalent circuit

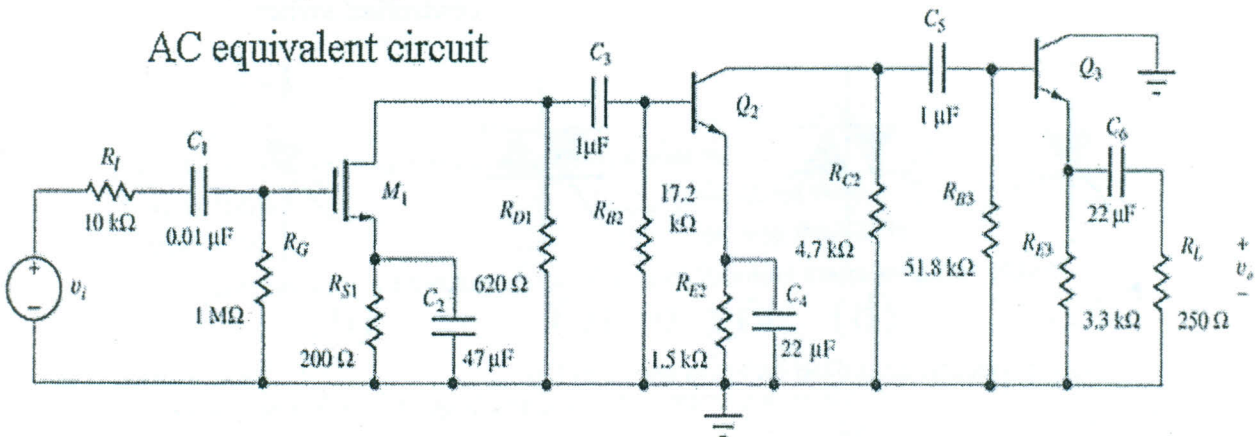


TABLE 17.3
 Transistor Parameters

	g_m	r_x	r_o	β_o	C_{GS}/C_x	C_{GD}/C_μ	r_x
M_1	10 mS	∞	12.2 k Ω	∞	5 pF	1 pF	0 Ω
Q_2	67.8 mS	2.39 k Ω	54.2 k Ω	150	39 pF	1 pF	250 Ω
Q_3	79.6 mS	1.00 k Ω	34.4 k Ω	80	50 pF	1 pF	250 Ω

TABLE 14.19
 Q-Points

	Q-POINT VALUES
M_1	(5.00 mA, 10.9 V)
Q_2	(1.57 mA, 5.09 V)
Q_3	(1.99 mA, 8.36 V)


the lower-cutoff frequency for a network having n coupling and bypass capacitors can be estimated from

$$\omega_L \cong \sum_{i=1}^n \frac{1}{R_{iS}C_i} \quad (17.33)$$

in which R_{iS} represents the resistance at the terminals of the i th capacitor C_i with all the other capacitors replaced by short circuits. The product $R_{iS}C_i$ represents the short-circuit time constant associated with capacitor C_i .

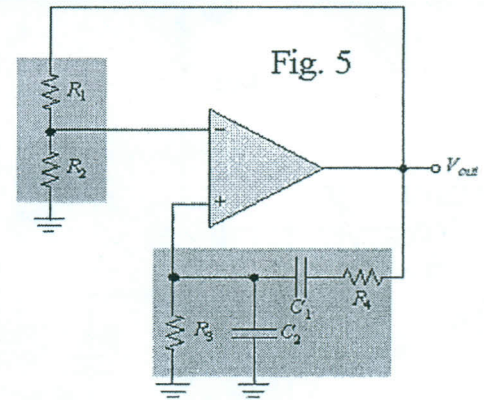Q21 Fig. 5 is

- ① Wien-Bridge Oscillator
- ② Phase-shift oscillator
- ③ Relaxation Oscillator
- ④ Hartley Oscillator




Q22 In a crystal oscillator, the crystal acts like a

- ① band-pass filter
- ② resonant circuit
- ③ notch filter
- ④ power source

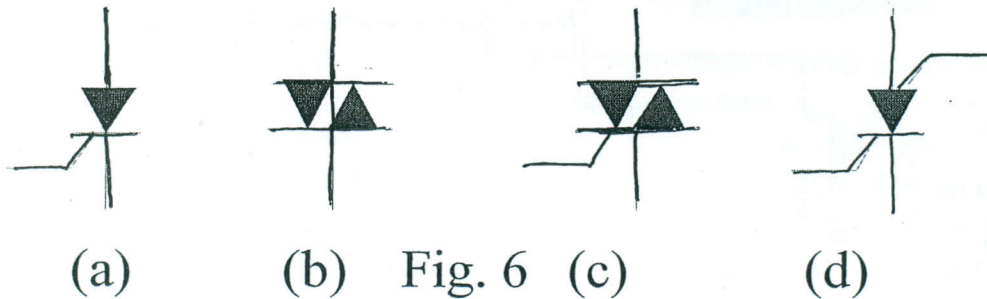Q23 A bidirectional thyristor is the

- ① 4-layer diode
- ② SCR
- ③ triac
- ④ silicon-controlled switch



Q24 The symbol for a silicon-controlled switch is shown in Fig.

- ① 6 (a)
- ② 6 (b)
- ③ 6 (c)
- ④ 6 (d)

Q25 A programmable unijunction transistor (PUT) is programmed by choosing the

- ① RC time constant
- ② gate resistors
- ③ power supply voltage
- ④ cathode resistor

Answer the following question:

(25 Marks)

R1 Using the Short-Circuit Time-Constant (SCTC) method:

For the multi-stage amplifier stage shown in the following figure

- a- Calculate R_{1S} , R_{2S} , R_{3S} , R_{4S} , R_{5S} , and R_{6S} in Ohms (12 Marks)
- b- Then estimate the lower cutoff frequency of the three-stage amplifier, ω_L (3 Marks)
- c- Repeat (a) for the same circuit after removing capacitors C_2 and C_4 (10 Marks)