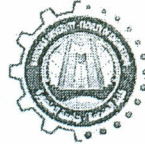




Mansoura university
Faculty of engineering
Electric Engineering Dept.



| | | |
|----------------------------------|---------------------|----------------------------|
| Course Title: Protection systems | Course Code: EE2423 | Year: 4 th year |
| Date: 5 /6/ 2013 | Allowed Time: 3 Hrs | Total Marks: 110 Marks |
| Second Term | Final Term Exam | No. of Pages: 3 |

Remarks: Answer All the following questions (assuming any missing data)

Question # 1 (20 Marks)

- (a) Describe with net sketch the operation of plunger type relay, and drive its force relation? (5 Marks)
- (b) Explain with the help of net diagram the construction and working of a solid-state time delay over current relay and its waveforms. (5 Marks)
- (c) What will be the torque equation of an induction type two input signals relay, if one flux is generated by voltage signal of $v = 220\sin(\omega t)$ across N_v turns with impedance of $1+j10 \Omega$ the other flux is generated by a current signals $i = 300 \sin(\omega t+50)$ through N_i turns. (10 Marks)

Question # 2 (20 Marks):

- (a) State the possible faults encountered in the oil immersed type reactor ? (5 Mark)
- (b) Draw the one line diagram showing a 200 hp motor connected to 4 kV bus. Assume the following bus and motor parameters:
- phase to phase fault current = 15000 A
 - three phase fault current = 25000A
 - ground fault current = 1500A
 - motor full load current = 25A
 - motor locked rotor current =150A
 - motor starting time = 1.5S
- select and set the phase and ground relays using time current characteristics shown in figure 2. (15 Marks)

Question # 3 (20 Marks):

- (a) What do you mean by Autorecloser and sectionalizer, what are the motivation of using them. (5 Marks)
- (b) For the radial system shown in Figure (1), Calculate;
- i. The CT's ratio at each bus. (5 Marks)

P.T.O

- ii. The time-delay overcurrent relay settings at each bus using the relay characteristic given in figure (2). (10 Marks)

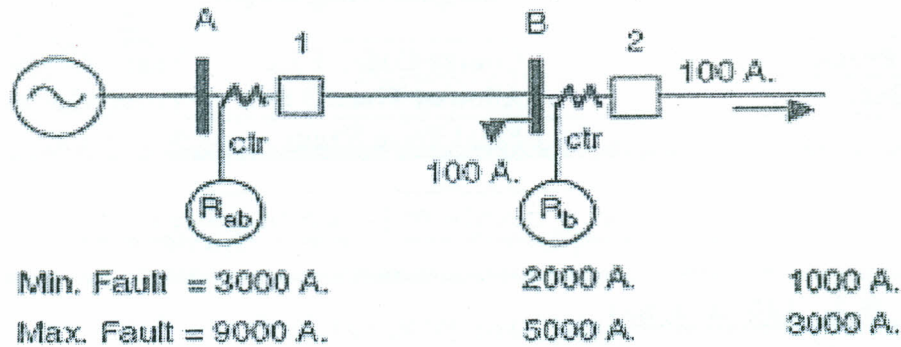


Figure (1)

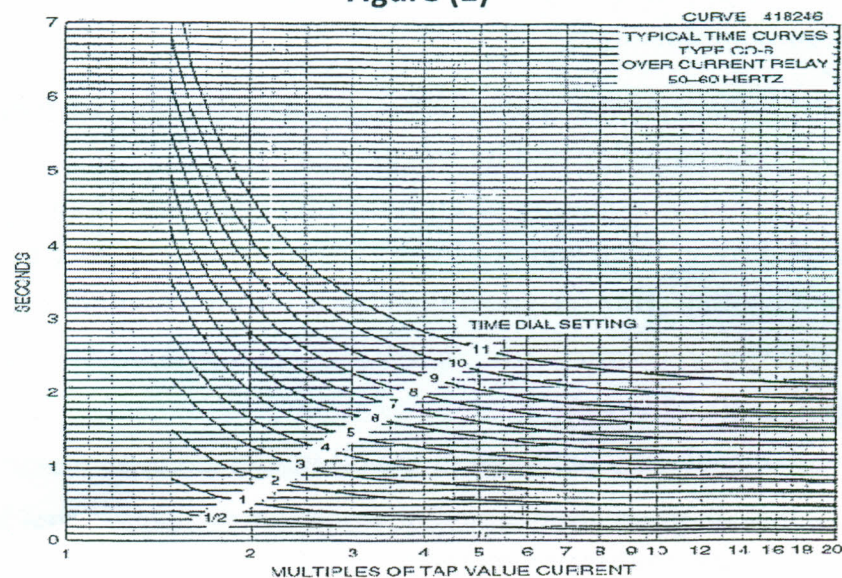


Figure (2)

Question # 4 (25 Marks):

- (a) A current transformer has the following data; 20 VA, class 10 P 20,1 amp. Evaluate an equivalent ANSI/IEEE standard current transformer to this current transformer. (5Marks)
- (b) Explain how to define the IEC and ANSI knee point for the protection CT? (5 Marks)
- (c) The system nominal voltage is 220 kV, and the positive sequence impedances for the various elements are given in the figure . The angle of maximum torque τ is 80° .the maximum load at relay site is 300MVA.
For an impedance relay R_{ab} in the system shown in the figure (3) determine the following:

P.T.O

- i. The CT and PT ratio for this relay?
- ii. The Rab relay side (secondary) zones setting? (5Marks)
- iii. Draw the relay Rab characteristics considering 10% offset in zone 3? (5 Marks)
- iv. The loadability limit for zone one of Rab relay, assuming a 0.85 power factor lag? (5 Marks)

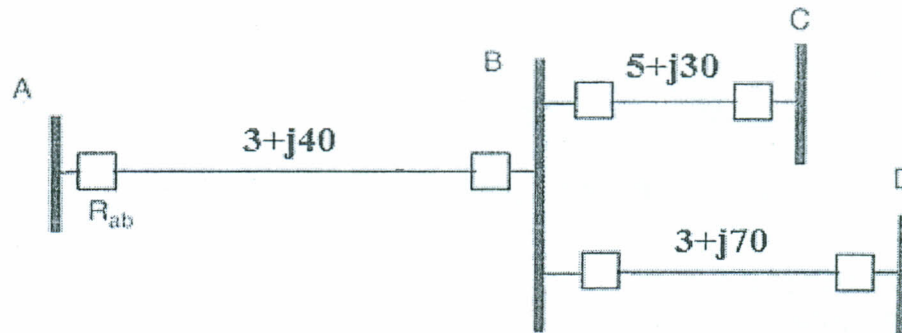


Figure (3)

Question # 5 (25 Mark)

- (a) State the factors which are affecting the accuracy of distance relays. (5 Marks)
- (b) A single phase transformer is rated at 110/69 kV, 100 MVA and. The 110 kV side has a tap changer with a range of 10%. Assume a maximum CT error of 5% in either of the two CTs.
 - i. Determine the CT ratios for a percentage differential relay to protect this transformer?
 - ii. If both relays windings are provided with taps for 3, 4, 4.3, 4.5, 4.8, 5, 5.2, 5.6, 5.7A, Determine the required slope of the relay characteristics?
 - iii. Draw the relay characteristics and what pickup current setting for the relay would you recommended? (20 Mark)

With Our Best Wishes

Dr/ Gabr M. Abdulsalam and Dr/A. Y. Hatata