

Answer All Questions:

1- Design an RC ramp generator to give an output that peaks as 5V. The supply voltage is 15V and the load to be connected with the output is $100\text{K}\Omega$. The ramp is to be triggered by a negative pulse of 3V, $\text{PW}=1\text{ms}$ and the space width of 1ms. The transistor is to be used is a normally ON and has $h_{FE\min}=50$. (15)

2- Design the constant current generator for the ramp generator in question (1) to produce linear ramp. Then design the circuit for adjusting the ramp amplitude from 3V to 5V. (15)

3- Design a transistor bootstrap ramp generator to provide an output amplitude of 5V over a time period of 1ms. The ramp is to be triggered by a negative pulse of 3V, pulse width of 1ms and the space width of 1ms. The circuit supplies a load of $1\text{K}\Omega$ and the ramp is to be linear within 2%. The supply voltage is $\pm 15\text{V}$, $h_{FE\min}=100$ for the transistor used. (15)

4- Design a free running ramp generator with an output frequency of 1Khz and an output amplitude in the range 0 V to 8 V. Use 741 operational amplifier and a supply voltage of $\pm 15\text{V}$. (15)